

Electrical Theory / Ohm's Law Quiz

Name _____

1. Another way of describing electromotive force (EMF) is the ____ of a circuit.


- (a) voltage
- (b) root mean square (rms)
- (c) potential difference
- (d) any of these

2. A way of describing the flow of electrons in a circuit is ____.

- (a) voltage
- (b) current
- (c) power
- (d) resistance


3. Conductor resistance varies with which of the following ?

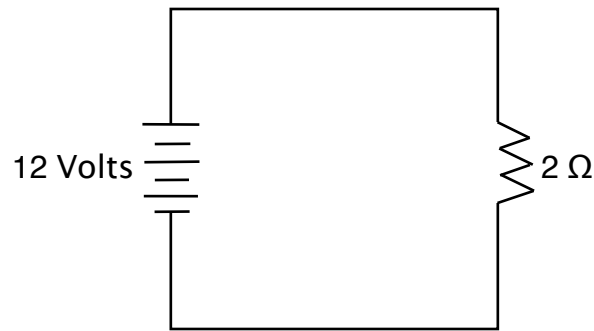- (a) material
- (b) voltage
- (c) current
- (d) power



4. The total current consumed in the circuit above equals ____ amps.

- (a) 72
- (b) 12
- (c) 6
- (d) 2

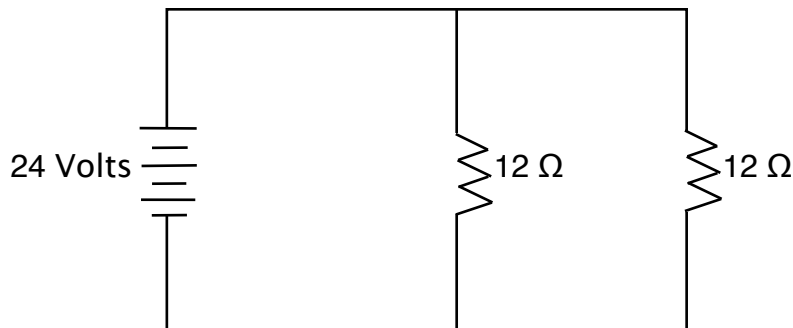


5. The total wattage consumed in the circuit above equals ____ watts.

- (a) 96
- (b) 24
- (c) 6
- (d) 4



6. The above circuit feeds a kitchen. The current passing through the circuit is _____ amps.

- (a) 183
- (b) 18.3
- (c) 13.3
- (d) 5

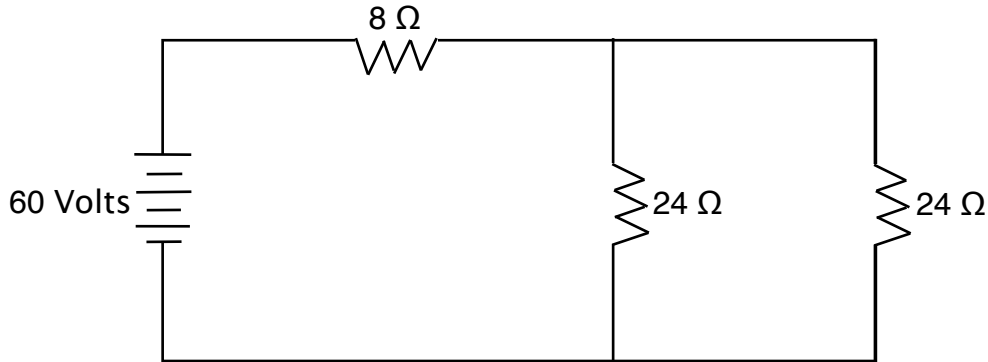

7. The wattage consumed at the $8\ \Omega$ resistor circuit above equals _____ volts.

- (a) 180
- (b) 108
- (c) 72
- (d) 60

8. If a blender is plugged into a 120 volt outlet that supplies 2.7 amps of current what amount of power (watts) is used by the blender ?

- (a) 324
- (b) 240
- (c) 120
- (d) 44.4

9. A 720 watt heater is rated at 240 volts, what would the wattage be if it was connected to a 230 volt source ?

- (a) 720
- (b) 691
- (c) 661
- (d) 80

10. What current flows through a hair dryer plugged into a 120 volt circuit with a resistance of 25 ohm's ?

- (a) 576
- (b) 528
- (c) 120
- (d) 4.8